

Amrit Singh
Analog Electronics - I
Assignment - 1.1.

Qn. 1

Applying KVL,

$$32 - 4I - (-8) - 2I = 0$$

$$32 - 4I + 8 - 2I = 0$$

$$40 - 6I = 0$$


$$6I = 40$$

$$I = \frac{40}{6} = 6.67A$$

$$V_1 = 4I = 4\Omega * 6.67A \\ = 26.67V$$

$$V_2 = -2\Omega * I = -2\Omega * 6.67A \\ = 13.33V \neq$$

Qn. 2.

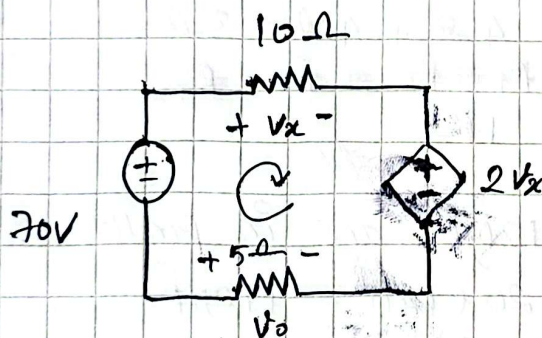

$$V_x = 10\Omega * I = 10I$$

$$V_0 = -5I$$

Using KVL,

$$-70 + V_x + 2V_x + V_0 = 0$$

$$-70 + 10I + 2(10I) + 5I = 0$$

$$-70 + 35I = 0$$

$$35I = 70$$

$$I = 2A$$

$$V_x = 20V$$

$$V_0 = -10I \neq$$

Qn. 3. $8\Omega, 10\Omega, 6\Omega$ are in series

$$R_1 = 8 + 10 + 6 = 24\Omega$$

R_1 is parallel with 12Ω resistor

$$R_2 = \frac{(24 \times 12)}{(24 + 12)} = 8\Omega$$

R_2 is ~~parallel~~ ^{series} with 4Ω

$$R_3 = (8 + 4)\Omega = 12\Omega \text{ resistor}$$

R_3 is parallel with 6Ω resistor

$$R_4 = \left(\frac{12 \times 6}{12 + 6} \right) = 4\Omega$$

So,

$$R_{eq} = \cancel{R_1 + R_2 + R_3 + R_4} = 4\Omega + 4\Omega + 3\Omega = 11\Omega$$

Qn. 4. \Rightarrow Here, $20\mu f$ & $120\mu f$ are in parallel.

$$C_1 = 20 + 120 = 140\mu f$$

$60\mu f$ capacitor is in series with $140\mu f$

i.e.

$$C_2 \Rightarrow \frac{60 \times 140}{60 + 140} = 42\mu f$$

$50\mu f$ & $70\mu f$ capacitors in parallel

$$C_3 = 50 + 70 = 120\mu f$$

C_2 ($42\mu f$) & C_3 ($120\mu f$) are in series.

$$C_{eq} = \frac{120 \times 42}{120 + 42} = 31.11\mu f$$

Qn. 5.

$$V_1 = V_{total} \times \frac{C_{bottom}}{C_{top} + C_{bottom}} = 150 \times \frac{20}{40 + 20}$$

$$V_1 = 50V$$

$$V_2 = V_{total} \times \frac{C_{top}}{C_{top} + C_{bottom}} = 150 \times \frac{40}{40 + 20} = 100V$$

$$V_3 = 150 \times \frac{30}{60 + 30} = 50V$$

$$V_4 = 150 \times \frac{60}{60 + 30} = 100V$$

Qn. 6

Series, $20H, 12H \& 10H \Rightarrow 42H$

$$42H \& 7H \text{ in parallel, } \Rightarrow \frac{7 \times 42H}{7 + 42} = 6H$$

Now, $6H$ is in series with $(4H \& 8H)$

$$L_{eq} = 4 + 6 + 8 = 18H$$

Qn. 7 $40mH \& 20mH$ are in series $\Rightarrow L_1 \Rightarrow 60mH$

L_1 is in parallel with $30mH$ inductor,

$$L_2 \Rightarrow \frac{30 \times 60}{30 + 60} = 20mH$$

$20mH$ is in series with $100mH$ inductor $\Rightarrow L_3 = 120mH$

$$120mH \text{ in parallel with } 40mH, L_4 = \frac{40 \times 120}{40 + 120} = 30mH$$

$30mH$ is in series with $20mH$, $L_5 = 20 + 30 = 50mH$

50mH is in parallel with 50mH

$$L_{eq} = \frac{50 \times 50}{50 + 50} = \frac{2500}{100} = 25mH$$